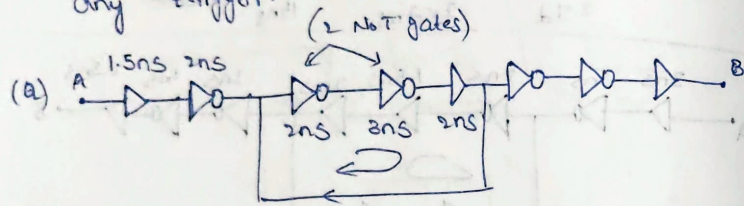


(\*) If the given loop has even no. of NOT gates in loop, then it is called as Monostable Multivibrator.

→ It'll have zero frequency, until you use any trigger:



A: Freq. = 0 (Even no. of inverters)  
(No oscillations)

⇒ DeMorgan's Theorem :-

1)  $\overline{A \cdot B} = \overline{A} + \overline{B}$

2)  $\overline{A+B} = \overline{A} \cdot \overline{B}$

★  $\overline{A+B+C} = \overline{A} \cdot \overline{B} \cdot \overline{C}$

★  $\overline{A \cdot B \cdot C} = \overline{A} + \overline{B} + \overline{C}$

END OF DAY 1

★ Important Points :-



→  $A \cdot 1 = A$  →  $A \cdot A = A$  →  $A + A = A$

→  $A \cdot 0 = 0$  →  $A \cdot \overline{A} = 0$  →  $A + 0 = A$

→  $A + 1 = 1$  →  $A + \overline{A} = 1$

⇒ Universal Gates DAY-2 (01-06-26)

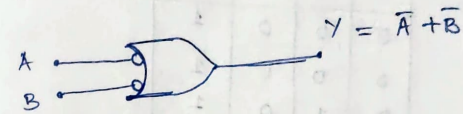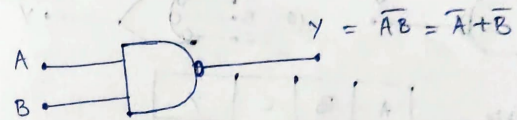⇒ NAND Gate :- Combination of AND + NOT gates




NAND = Bubbled OR gate.

Truth Table -


| A | B | Y |
|---|---|---|
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 0 | 0 | 1 |
| 1 | 1 | 0 |

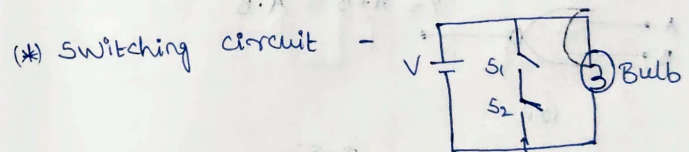O/P is low, if both inputs are high. Else all cases are High.



Truth Table -

| S <sub>1</sub> | S <sub>2</sub> | Bulb |
|----------------|----------------|------|
| ON             | OFF            | ON   |
| OFF            | ON             | ON   |
| OFF            | OFF            | ON   |
| ON             | ON             | OFF  |

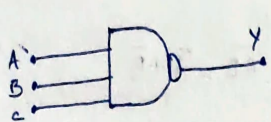


Truth Table -

| A | B | C | Y |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |



⇒ If both I/P's are low, o/p will be High.


(\*) Switching circuit -

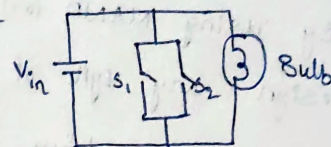



Truth Table -

| S <sub>1</sub> | S <sub>2</sub> | Bulb |
|----------------|----------------|------|
| ON             | OFF            | OFF  |
| OFF            | ON             | OFF  |
| OFF            | OFF            | ON   |
| ON             | ON             | OFF  |

(\*) 3 I/P's NOR Gate

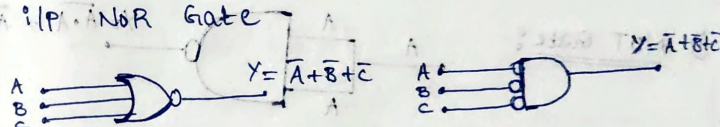

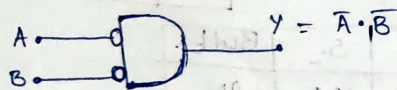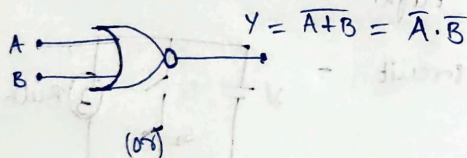⇒ NOR Gate :- Combination of (OR + NOT) gates.



NOR = Bubbled AND gate

Truth Table -

| A | B | Y |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

Truth Table -

| A | B | C | Y |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |




## → WHY Universal gates :-

→ By using NAND (or) NOR gates, you can design any type of gate.  
→ That's why they are called Universal gates.


→ Also, you can implement any gate using NAND (or) NOR gates.

## (\*) NAND Gate as universal gate :-


### ① NOT Gate :-

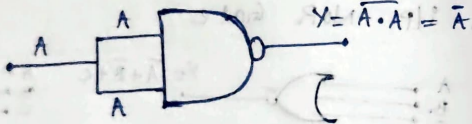

### ② AND Gate :-

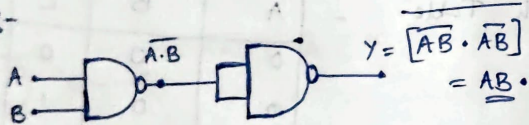


### ③ OR Gate :-

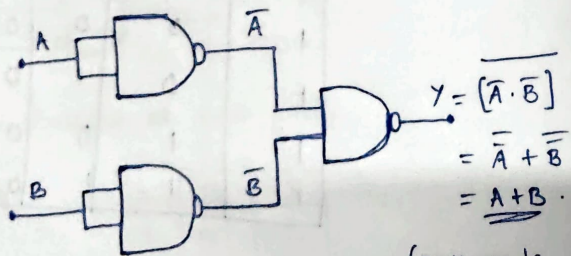


(DeMorgan's Law)

## (\*) NOR gate as universal gate :-


### ① NOT gate :-

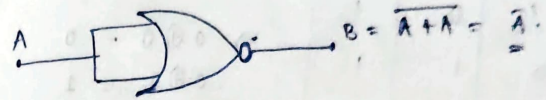

### ② OR gate :-

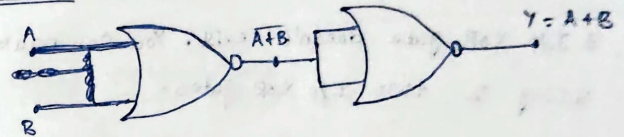

### ③ AND Gate :-

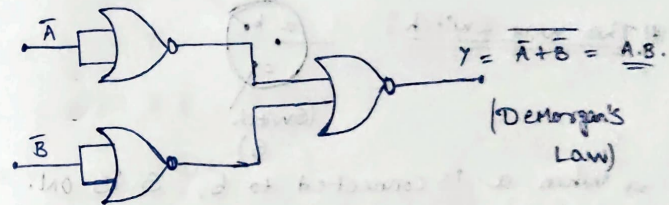

## ⇒ Arithmetic Gates :-

① EX-OR / XOR gates :- op is High when both I/P are different. op is Low when both I/P are same.



$$AB = BA$$

$$A + B = B + A$$


| A | B | $\bar{A}$ | $\bar{B}$ | Y |
|---|---|-----------|-----------|---|
| 0 | 0 | 1         | 1         | 0 |
| 0 | 1 | 1         | 0         | 1 |
| 1 | 0 | 0         | 1         | 1 |
| 1 | 1 | 0         | 0         | 0 |

Truth Table


$$\begin{aligned} 0 \oplus 0 &= 0 \\ 0 \oplus 1 &= 1 \\ 1 \oplus 0 &= 1 \\ 1 \oplus 1 &= 0 \end{aligned}$$

Note: 3 I/p XOR gate doesn't exist. You can make it using 2 two I/p XOR gates.

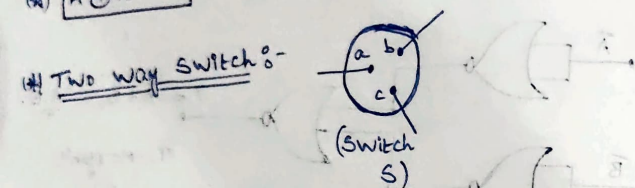(\*)  $A \oplus \bar{A} = 1 \Rightarrow$  XOR gate = odd no. of 1's detector



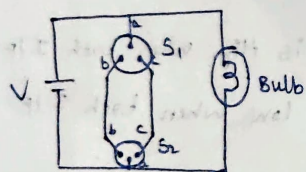$\Rightarrow$  When a is connected to b, S is ON.  
When a is connected to c, S is OFF.




| $S_1$ | $S_2$ | Bulb |
|-------|-------|------|
| ON    | ON    | OFF  |
| ON    | OFF   | ON   |
| OFF   | ON    | ON   |
| OFF   | OFF   | OFF  |

$$\Rightarrow A \oplus B = B \oplus A$$

$$\Rightarrow A \oplus B \oplus C = (A \oplus B) \oplus C = \underline{A \oplus (B \oplus C)}$$

XOR gate from Basic gates:-

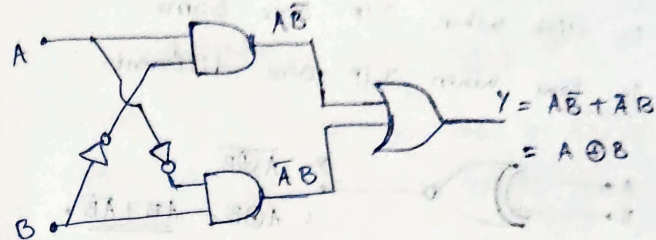

Important Observations:-

$$① A \oplus A = A\bar{A} + \bar{A}A = 0$$

$$② A \oplus 0 = A \cdot 1 + \bar{A} \cdot 0 = A$$

$$③ A \oplus 1 = A \cdot 0 + \bar{A} \cdot 1 = \bar{A}$$

$$④ A \oplus \bar{A} = A \cdot A + \bar{A} \cdot \bar{A} = A + \bar{A} = 1$$

$$\begin{aligned} ⑤ A \oplus B = C \quad ; \quad A \oplus C &= ? \quad \Rightarrow B \oplus C = \underline{A} \\ &= A \oplus (A \oplus B) \\ &= 0 \oplus B = \underline{B} \end{aligned}$$

(a) Find

$$\begin{aligned} ① A \oplus A \oplus A \oplus A &= (\bar{A} + A) \oplus (\bar{A} + A) \\ &= 0 \oplus 0 = \underline{0} \end{aligned}$$

$$② A \oplus A \oplus A \oplus A \oplus A \oplus A = \underline{0}$$

$$③ A \oplus A \oplus A = 0 \oplus A = \underline{A}$$

$$④ A \oplus A \oplus A \oplus A \oplus A = \underline{A}$$


$\Rightarrow$  Even no. of A's = 0  $\Rightarrow$  odd no. of A's = A



⇒ EXNOR (or) XNOR :- [XOR + NOT]

o/p is High when I/p are Same.

o/p is Low when I/p are different.

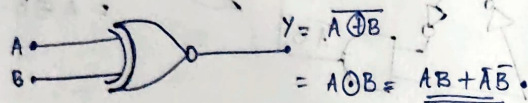

| A | B | $\bar{A}$ | $\bar{B}$ | Y |
|---|---|-----------|-----------|---|
| 0 | 0 | 1         | 1         | 1 |
| 0 | 1 | 1         | 0         | 0 |
| 1 | 0 | 0         | 1         | 0 |
| 1 | 1 | 0         | 0         | 1 |

⇒ (Equivalence detector)

⇒ Solve:-

① 10101 = 1      ③ 00000 = 0

② 101010101 = 1      ④ 0000000 = 0

⑤ 100000100 = 0      ⑥ 100010001 = 1

(★) XOR Gate = odd no. of 1's detector  
 XNOR Gate = even no. of 0's detector

⇒ odd no. of 0's = 0

Even no. of 0's = 1

(Shortcut)


★  $A \oplus B = \overline{A \odot B}$

$A \oplus B \oplus C = \overline{A \odot B \odot C}$

⇒ For even no. of I/p ⇒ XOR = XNOR

odd " " " ⇒ XOR =  $\overline{\text{XNOR}}$

(★) Switching CKT

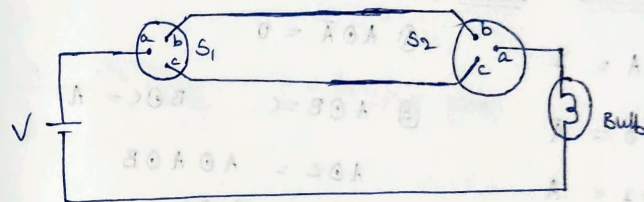


| $S_1$ | $S_2$ | Bulb |
|-------|-------|------|
| ON    | ON    | ON   |
| ON    | OFF   | OFF  |
| OFF   | ON    | OFF  |
| OFF   | OFF   | ON   |

⇒  $A \odot B = B \odot A$

⇒  $A \odot (B \odot C) = (A \odot B) \odot C$

⇒ XNOR using other gates :-

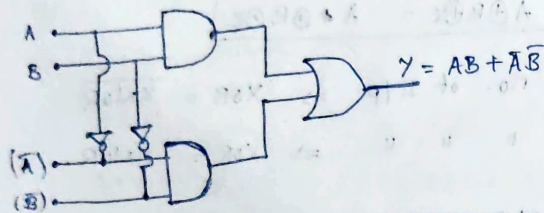

⇒ Important observations :-

①  $A \odot A = 1$

④  $A \odot \bar{A} = 0$

②  $A \odot 0 = \bar{A}$

③  $A \odot B = C, \quad B \odot C = A$

③  $A \odot 1 = \bar{A}$

$A \odot C = A \odot A \odot B$

$= 1 \odot B = B$

(Q) Find

①  $A \odot A \odot A = A$

②  $A \odot A = 1$

③  $A \odot A \odot A \odot A = 1$




④  $A \odot A \odot A \odot A \odot A = A$

Even no. of A = 1



odd " " " = A

|       |       |       |
|-------|-------|-------|
| 1 1 0 | 1 1 0 | 1 1 0 |
| 1 1 0 | 1 1 0 | 1 1 0 |
| 1 1 0 | 1 1 0 | 1 1 0 |


⇒ Buffer, NOT gates using XOR, XNOR :-

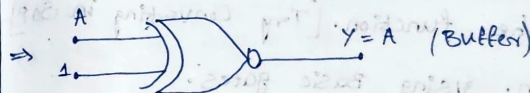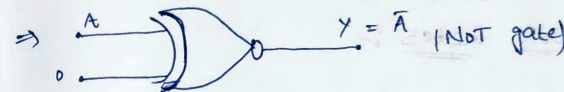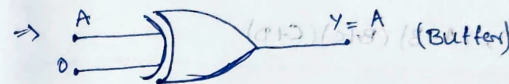

⇒ Equivalent Gates :-

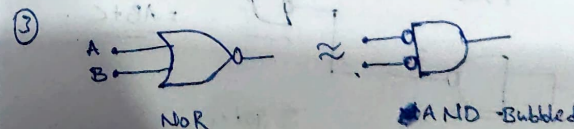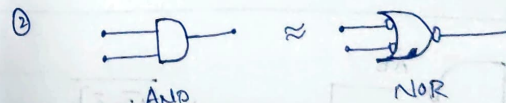



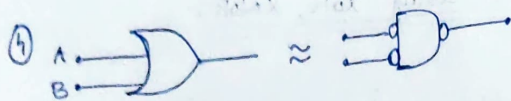

(\*) Sum of Product [SOP] & Product of Sum [POS]

① SOP:-  $AB + CD, AB + BC + CD$

② POS:-  $(A+B)(C+D), (A+B)(B+C)(C+D)$

⇒ Implementation using Min. no. of 2 I/p

NAND (or) NOR Gates:-

⇒ Min. no. of NAND Gate:-

① Minimize the function. [Try Converting in SOP]

② Implement fn. using basic gates.

③ Convert Basic gates to NAND gates.


No. of NAND gates

NOT - 1


AND - 2

OR - 3


(Q)  $AB + C$

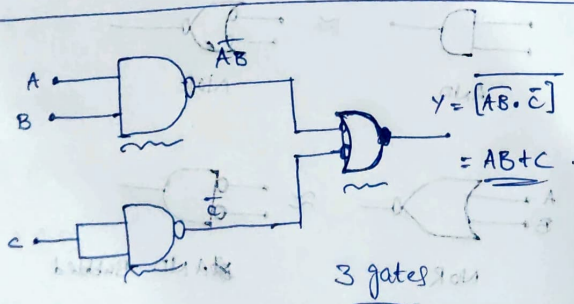

(Q)  $AB + CD$

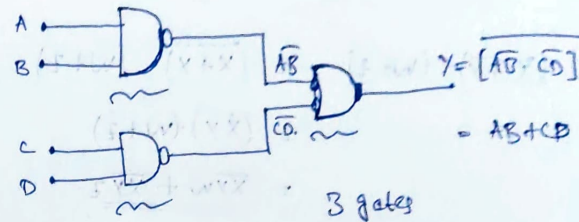


(Q)  $AB + BC + CD$

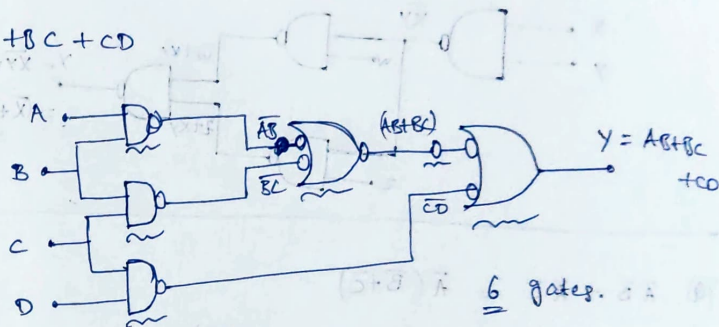


(Q)  $AB + BC + CD + DA = (A+C)B + (A+C)D$


$= (B+D)(A+C)$

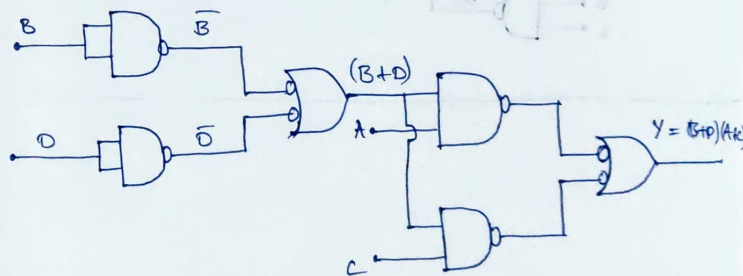


(Q)  $ABCD$

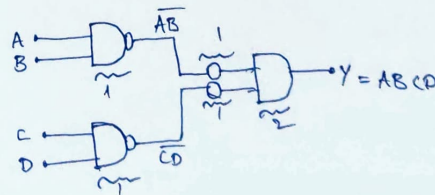
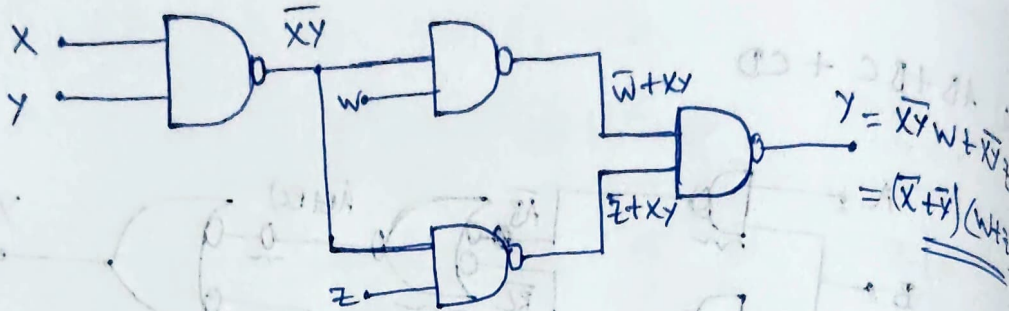
$$\begin{aligned}
 (Q) \quad (\bar{x} + \bar{y}) \cdot (w + z) &= \overline{(x + y)} \cdot (w + z) \\
 &= \overline{(xy)} \cdot (w + z) \\
 &= \underline{\underline{\bar{x}\bar{y}w + \bar{x}\bar{y}z}}
 \end{aligned}$$


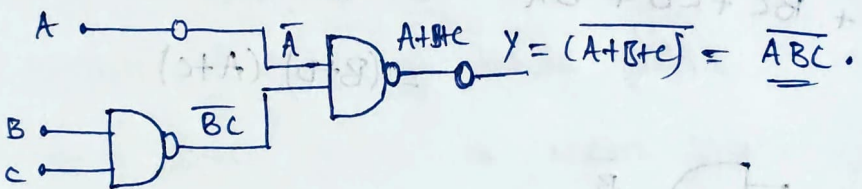
$$\begin{aligned}
 (Q) \quad \bar{A}\bar{B} + \bar{A}\bar{C} &= \bar{A}(\bar{B} + \bar{C}) \\
 &= \bar{A}(\overline{B+C}) = \underline{\underline{\bar{A}(\overline{BC})}}
 \end{aligned}$$



END OF  
DAY 2 //